

CSARCH1

Design Problem: Euler's Totient Function Counter

This is an individual exercise. Discussion between peers is allowed but showing of codes and circuit verse design will be considered cheating.

[Euler's totient function](#) (phi function), denoted as $\phi(n)$, is a function that counts the number of positive integers less than or equal to n that are relatively prime to n . Euler's totient function is used in various algorithms in particular, the RSA algorithm used in cryptography.

You need to design a circuit that calculates Euler's totient function for the first 16 numbers and displays the results on a 7-segment display. The BCD display will change to the next number at the rising edge of the clock. The first 16 numbers of the Euler's totient function are [1,1,2,2,4,2,6,4,6,4,10,4,12,6,8,8]. Display 10 and 12 as A and C. so the display should be [1,1,2,2,4,2,6,4,6,4, A, C, 6,8,8]. It will then repeat, showing the pattern again. An input R=1, resets the sequence to the first element. Provide an output for your 7-segment as A, B,C, D, E, F, G, similar to the Design Exercise 1.



Grading System:

- Running Verilog Design [80%]
- Documentation [20%]
- Bonus 20 points: Instead of going back immediately from the first display, it will display them first, reverse, and then repeat the pattern again. Example: [1,1,2,2,4,2,6,4,6,4,A,C,6,8,8,8,6,C,4,A,4,6,4,6,2,4,2,2,1,1]

Testbench:

```
`timescale 1ns / 1ps

module TestBench();
    reg R, clk_0;
    wire A, B, C, D, E, F, G;

    EulerTotient DUT0(R, clk_0, A, B, C, D, E, F, G);

    always begin
        clk_0 = 0;
        forever #1000 clk_0 = ~clk_0;
    end

    always @(posedge clk_0) begin
        R=0;
        #100
        R=1;
        #2000
        $display("R=%b clk_0=%b ABCDEFG = %b%b%b%b%b%b%b", R, clk_0, A, B, C, D, E, F, G); // 1
        #2000
        $display("R=%b clk_0=%b ABCDEFG = %b%b%b%b%b%b%b", R, clk_0, A, B, C, D, E, F, G); // 1
        #2000
        $display("R=%b clk_0=%b ABCDEFG = %b%b%b%b%b%b%b", R, clk_0, A, B, C, D, E, F, G); // 1
        R=0;
        #2000
        $display("R=%b clk_0=%b ABCDEFG = %b%b%b%b%b%b%b", R, clk_0, A, B, C, D, E, F, G); // 1
        #2000
        $display("R=%b clk_0=%b ABCDEFG = %b%b%b%b%b%b%b", R, clk_0, A, B, C, D, E, F, G); // 2
        #2000
        $display("R=%b clk_0=%b ABCDEFG = %b%b%b%b%b%b%b", R, clk_0, A, B, C, D, E, F, G); // 2
        #2000
        $display("R=%b clk_0=%b ABCDEFG = %b%b%b%b%b%b%b", R, clk_0, A, B, C, D, E, F, G); // 4
        #2000
        $display("R=%b clk_0=%b ABCDEFG = %b%b%b%b%b%b%b", R, clk_0, A, B, C, D, E, F, G); // 2
        #2000
        $display("R=%b clk_0=%b ABCDEFG = %b%b%b%b%b%b%b", R, clk_0, A, B, C, D, E, F, G); // 6
        #2000
        $display("R=%b clk_0=%b ABCDEFG = %b%b%b%b%b%b%b", R, clk_0, A, B, C, D, E, F, G); // 4

        /*add more tests as needed*/
    $finish;
    end

endmodule
```